

$$x(t) = e^{-\frac{\Gamma}{2}t} \left(x_0 \cos(\omega_d t) + b \sin(\omega_d t) \right)$$

$$b = \frac{v_0 - \frac{\Gamma}{2} x_0}{\omega_d}$$

$$\omega_d = \sqrt{\omega^2 - \frac{\Gamma^2}{4}}$$

$$\Gamma = \frac{b}{m}$$

no damping

$$x(t) = x_0 \cos(\omega t) + \frac{v_0}{\omega} \sin(\omega t)$$

$$\omega = \sqrt{\frac{k}{m}}$$

$$\omega_d = \sqrt{\omega^2 - \frac{\Gamma^2}{4}}$$

damping term

$$\lim_{\Gamma \rightarrow 0} \omega_d = \sqrt{\omega^2} = \omega$$

$$\omega_d = \omega$$

what happens $\Gamma \rightarrow 0$

Damped solⁿ : $\Gamma \rightarrow 0$

$$x(t) = e^{-\frac{\Gamma}{2}t} \left(x_0 \cos(\omega_d t) + b \sin(\omega_d t) \right)$$

$$x(t) = x_0 \cos(\omega t) + \frac{v_0}{\omega} \sin(\omega t)$$

$$b = \frac{v_0 - \frac{\Gamma}{2} x_0}{\omega_d}$$

$$b = \frac{v_0}{\omega_d} = \frac{v_0}{\omega}$$

$$F = m \ddot{x}$$

$$-kx - b\dot{x} = m \ddot{x}$$

[N] [N] [N]

$$[N] = \left[\frac{kg \cdot m}{s^2} \right]$$

$$F = m a$$

$$[kg] \left[\frac{m}{s^2} \right]$$

$$F \rightarrow \left[\frac{kg \cdot m}{s^2} \right]$$

$$b \dot{x}$$



velocity $\frac{dx}{dt}$

$$\left[\frac{kg}{s} \right] \left[\frac{m}{s} \right]
$$b \rightarrow \text{units of } \frac{kg}{s}$$$$



$[\frac{1}{s^2}]$

Mechanics

Simple Harmonic Motion

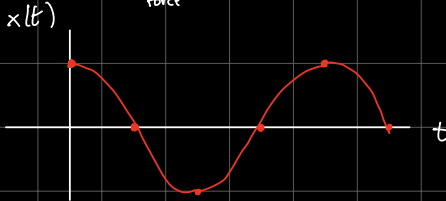
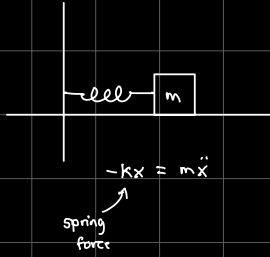


Damped Harmonic Motion

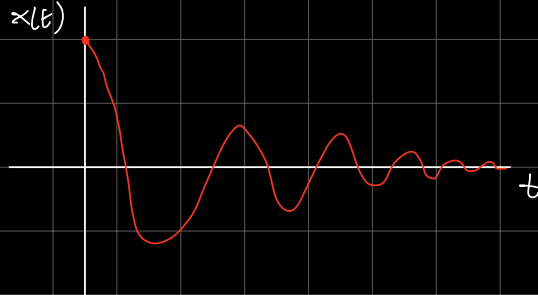
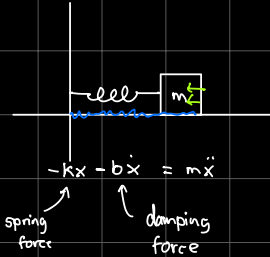


Circuits


SHM: LC Circuit

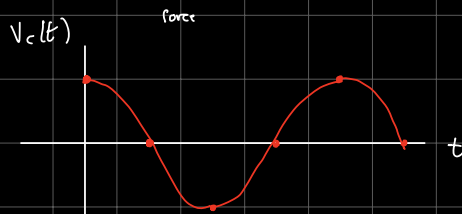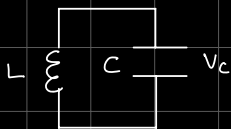

DHM: RLC Circuit

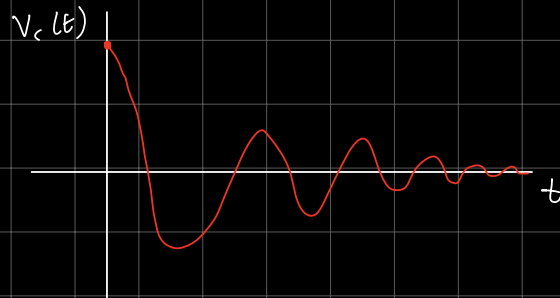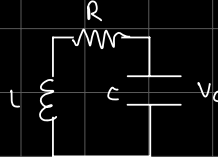

Goal: RC circuit

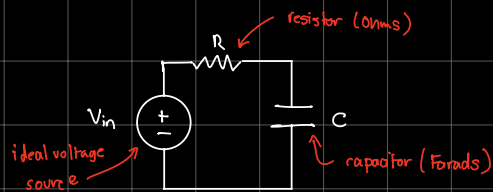

Voltage, Current, & Resistance


1) Current $i(t)$ units: amps

- flow of charge particles (in a wire) $\frac{dQ}{dt}$ ← electric charge (+, -)





2) Resistance R (ohms)

- opposes current, dissipates energy

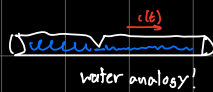


3) Voltage

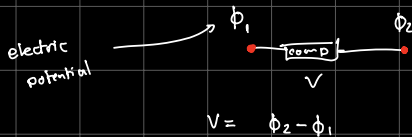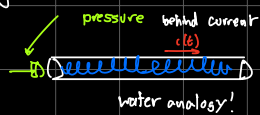

Device law: how do we relate voltage across & current through


- Resistor

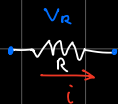

$$V_R = iR \text{ (Ohm's law)}$$


- Capacitor

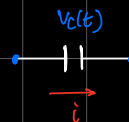↳ store electric charge → $q(t)$
 ↳ capacitance $C = \frac{Q}{V}$ ← electric charge
 $VC = Q$ ← voltage




$$i = C \frac{dV_C(t)}{dt}$$

Kirchoff's Voltage Law (Loop Rule)

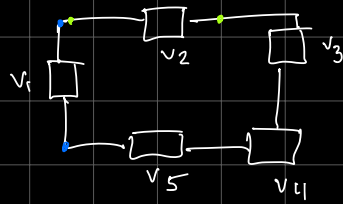

$$V_1 + V_2 + V_3 + V_4 + V_5 = 0$$

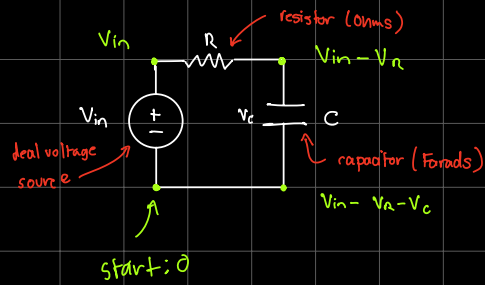

Walk around circuit

$$0 = V_{in} + V_R + V_C$$

↑
positive

$$0 = V_{in} - iR - V_C$$

$$i = C \frac{dV_C}{dt}$$

$$0 = V_{in} - RC \frac{dV_C}{dt} - V_C$$

$$V_{in} = \underline{V_C} + RC \frac{dV_C}{dt} \quad \leftarrow \text{1st order}$$

↑
Solve for V_C
inhomogeneous DE

$$0 = \omega^2 \underline{x} + \underline{\ddot{x}} \quad \leftarrow \text{2nd order}$$

↑
Solve for x
homogeneous DE



$$V_C(t) = V_{in} + C_1 e^{-\frac{t}{RC}}$$

$$V_C(t=0) = V_{in} + C_1 = V_0 \quad \leftarrow \text{initial voltage in cap}$$

$$C_1 = V_0 - V_{in}$$

$$V_C(t) = V_{in} + (V_0 - V_{in}) e^{-\frac{t}{RC}}$$