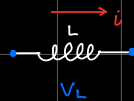


Goal: LC Circuit


- example of simple harmonic oscillator
 - what is it that's oscillating? Current and Voltage

Inductors: also store energy, like capacitors, but they do so in the magnetic field

- usually cylindrical windings of wire
- 'inductance' L in Henries (H)
- device law:


$$V_L = L \frac{di}{dt}$$

Solving LC Circuit:

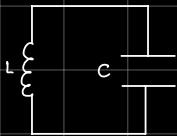


KVL: $V_L + V_C = 0$

$$L \frac{di}{dt} + V_C = 0$$

Recall $i = C \frac{dV_C}{dt}$ (device law, capacitors)

$$LC \frac{d^2 V_C}{dt^2} + V_C = 0$$

$$\frac{d^2 V_C}{dt^2} + \frac{1}{LC} V_C = 0 \quad \longleftrightarrow \quad \frac{d^2 x}{dt^2} + \omega^2 x = 0$$

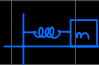analogous to 

* See 'SHO Solution Derivation' in lesson 1 *

Solⁿ form: $V_C(t) = A \cos(\omega t) + B \sin(\omega t)$

$$-A\omega^2 \cos(\omega t) - B\omega^2 \sin(\omega t) + \frac{1}{LC} [A \cos(\omega t) + B \sin(\omega t)] = 0$$

$$\frac{1}{LC} [A \cos(\omega t) + B \sin(\omega t)] = \omega^2 [A \cos(\omega t) + B \sin(\omega t)]$$

$$\omega = \frac{1}{\sqrt{LC}}$$

- To solve for A & B , we use the initial conditions $V_C(t=0) = V_0$ and $i(t=0) = i_0$

$$V_C(t=0) = A = V_0$$


$$i(t) = C \frac{dV_C}{dt} = C [-A\omega \sin(\omega t) + B\omega \cos(\omega t)]$$

$$i(t=0) = CB\omega = i_0, \quad B = \frac{i_0}{\omega C} = \frac{i_0 \sqrt{LC}}{C} = i_0 \sqrt{\frac{L}{C}}$$


$$V_C(t) = V_0 \cos\left(\frac{t}{\sqrt{LC}}\right) + i_0 \sqrt{\frac{L}{C}} \sin\left(\frac{t}{\sqrt{LC}}\right)$$

LC Circuit

1)


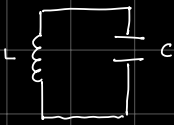


$$v_c(t) = \dots$$

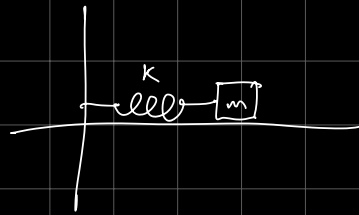


RLC Circuit


2)

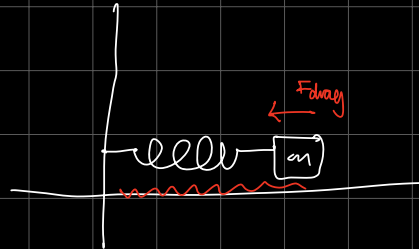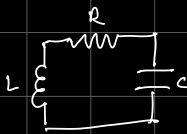

1) LC Circuit

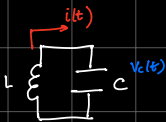

- Inductor / solenoid

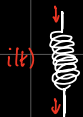

store energy (current)
in the magnetic
field




device law:

$$v_L = -L \frac{di(t)}{dt}$$

- capacitor





store energy
electric field

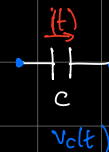

device law

$$i(t) = C \frac{dv_c(t)}{dt}$$

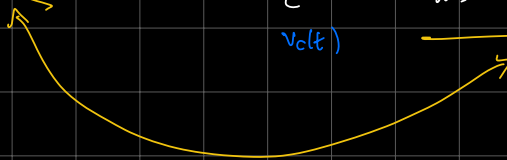

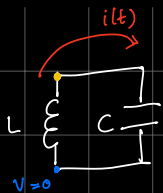

$$v_L + v_C = 0$$

$$-L \frac{di(t)}{dt} - v_C = 0$$

Device cap: $i(t) = C \frac{dv_C}{dt}$

$$-L \frac{d}{dt} \left[C \frac{dv_C}{dt} \right] - v_C = 0$$

$$-LC \frac{d^2 v_C}{dt^2} - v_C = 0$$

↓

$$\frac{d^2 v_C}{dt^2} + \frac{1}{LC} v_C = 0$$

standard form

~~derivative~~

$$\frac{d^2 v_C}{dt^2} + \frac{1}{LC} v_C = 0$$

$$\longleftrightarrow \frac{d^2 x}{dt^2} + \frac{k}{m} x = 0$$

guess $x(t) = A \sin(\omega t) + B \cos(\omega t)$

$\frac{d^2}{dt^2}$

guess: $v_C(t) = A \sin(\omega t) + B \cos(\omega t)$

$$\frac{dv_C}{dt} = A \omega \cos(\omega t) - B \omega \sin(\omega t)$$

$$\frac{d^2 v_C}{dt^2} = -A \omega^2 \sin(\omega t) - B \omega^2 \cos(\omega t)$$

$$-A \omega^2 \sin(\omega t) - B \omega^2 \cos(\omega t) + \frac{1}{LC} (A \sin(\omega t) + B \cos(\omega t)) = 0$$

$$\frac{1}{LC} (A \sin(\omega t) + B \cos(\omega t)) = A \omega^2 \sin(\omega t) + B \omega^2 \cos(\omega t)$$

$$\frac{1}{LC} (A \sin(\omega t) + B \cos(\omega t)) = \omega^2 (A \sin(\omega t) + B \cos(\omega t))$$

$$\frac{1}{LC} = \omega^2$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$v_c(t) = A \sin(\omega t) + B \cos(\omega t)$$

$$\omega = \frac{1}{\sqrt{LC}}$$

$$\frac{1.000 \text{ [m]}}{1.000 \text{ [m]}}$$

$$\omega = \sqrt{\frac{1}{LC}}$$

$$\frac{x_0}{V_0}$$

$$V_0 = v_c(t=0) = ?$$

$$i_0 = i(t=0) = ?$$

$$v_c(t=0) = V_0 = B$$

$$v_c(t) = A \sin(\omega t) + V_0 \cos(\omega t)$$

$$\text{device law } i(t) = C \frac{dv_c(t)}{dt}$$

$$i(t) = C \left(A \omega \cos(\omega t) - V_0 \omega \sin(\omega t) \right)$$

$$i(t=0) = C (A \omega + 0) = i_0$$

$$i_0 = C \omega A$$

$$A = \frac{i_0}{C \omega}$$

master eq.:

$$v_c(t) = \frac{i_0}{C \omega} \sin(\omega t) + V_0 \cos(\omega t), \quad \omega = \frac{1}{\sqrt{LC}}$$

$$\begin{aligned} i(t) &= C \frac{dv_c(t)}{dt} = C \frac{d}{dt} \left[\frac{i_0}{C \omega} \sin(\omega t) + V_0 \cos(\omega t) \right] \\ &= C \left[\frac{i_0}{C} \cos(\omega t) - V_0 \omega \sin(\omega t) \right] \end{aligned}$$

$$i(t) = i_0 \cos(\omega t) - V_0 \omega C \sin(\omega t)$$




How is the energy moving around in this circuit?

oscillates

$$E_{\text{tot}} = E_C + E_L$$

$$E_C = \frac{1}{2} C V_c(t)^2$$

$$E_L = \frac{1}{2} L i(t)^2$$

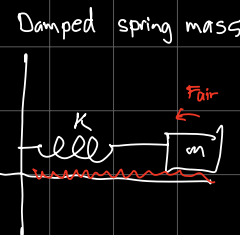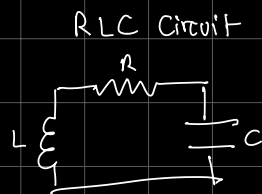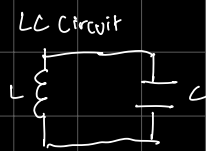

Can we use "Damped spring mass - sys" to solve RLC

RLC

KVL: $V_L + V_R + V_C = 0$

$$-L \frac{di(t)}{dt} - i(t)R - V_C = 0$$

$$i(t) = C \frac{dV_C}{dt}$$

$$-LC \frac{d^2 V_C}{dt^2} - RC \frac{dV_C}{dt} - V_C = 0$$

$$LC \frac{d^2 V_C}{dt^2} + RC \frac{dV_C}{dt} + V_C = 0$$

$$\frac{d^2 V_C}{dt^2} + \frac{R}{L} \frac{dV_C}{dt} + \frac{1}{LC} V_C = 0$$

Damped spring mass

$F = ma$

$$F_s + F_{damp} = m \frac{d^2 x}{dt^2}$$

$$-Kx - b \frac{dx}{dt} = m \frac{d^2 x}{dt^2}$$

$$m \frac{d^2 x}{dt^2} + b \frac{dx}{dt} + Kx = 0$$

$$\frac{d^2 x}{dt^2} + \frac{b}{m} \frac{dx}{dt} + \frac{K}{m} x = 0$$

Solⁿ

$$V_C(t) = e^{-\frac{R}{2L}t} \left(V_0 \cos(\omega_d t) + \gamma \sin(\omega_d t) \right)$$

$$x(t) = e^{-\frac{\Gamma}{2}t} \left(x_0 \cos(\omega_d t) + \gamma \sin(\omega_d t) \right)$$

$$\omega_d = \sqrt{\omega^2 - \frac{1}{4} \left(\frac{R}{L} \right)^2}, \quad \omega = \frac{1}{\sqrt{LC}}$$

$$\gamma = \frac{i_0 - \frac{R}{2L} V_0}{\omega_d}$$

$$\gamma = \frac{V_0 - \frac{\Gamma}{2} x_0}{\omega_d}$$

$$\omega_d = \sqrt{\omega^2 - \frac{\Gamma^2}{4}}$$

$$\Gamma = \frac{b}{m}$$